

Physical Science: Ohm's Law Practice Name _____ Per _____

Solve the following problems. Show all your work and use correct units.

Formulas: $I = V/R$ $V = IR$ $R = V/I$
I = current in Amperes (A) V = Voltage in Volts (V) R = Resistance in ohms (Ω)

1. How much current would flow through a circuit that has 1000 ohms of resistance if powered by 1.5 volts?
2. How many amperes of current will flow through a circuit that has 3 ohms of resistance if powered by a 12 volt battery?
3. The side lights of a car have 10 ohms of resistance. How much current will a 12 volt battery create through the lights?
4. What is the current in the 30 ohm heating coil of a coffee maker that operates on a 120 volt circuit?
5. How much resistance allows 6 V battery to produce a current of 0.006 A?
6. What is the resistance of a curling iron that draws 12 A of current on a 120 V circuit?

